

# **CprE 2810: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# State Minimization

*CprE 2810: Digital Logic*  
*Iowa State University, Ames, IA*  
*Copyright © Alexander Stoytchev*

# **Administrative Stuff**

- **Homework 11 is due on Monday Nov 17 @ 10pm**
- **Homework 12 will be due on Monday Dec 1 @ 10pm**


# Equivalence of states

“Two states  $S_i$  and  $S_j$  are said to be equivalent if and only if for every possible input sequence, the same output sequence will be produced regardless of whether  $S_i$  or  $S_j$  is the initial state.”

# **Partition Minimization Procedure**
 
# 0-successor


Assuming that we have only one input signal  $w$



$S_2$  is a 0-successor of  $S_1$
 
# 0-successor

Assuming that we have only one input signal  $w$




$S_2$  is a 0-successor of  $S_1$

$S_2$  is a 0-successor of  $S_5$
 
# 1-successor

Assuming that we have only one input signal  $w$




$S_4$  is a 1-successor of  $S_3$


 
# 1-successor

Assuming that we have only one input signal  $w$




$S_4$  is a 1-successor of  $S_3$

$S_4$  is a 1-successor of  $S_6$
 
# 1-successor

Assuming that we have only one input signal  $w$



$S_4$  is a 1-successor of  $S_3$

$S_4$  is a 1-successor of  $S_6$

$S_7$  is a 1-successor of  $S_4$


## **k-successors of a State**

**Assuming that we have only one input signal  $w$ ,  
then  $k$  can only be equal to 0 or 1.**
 
# k-successors of a State

Assuming that we have only one input signal  $w$ , then  $k$  can only be equal to 0 or 1.

In other words, this is the familiar 0-successor or 1-successor case.



$S_2$  is a 0-successor of  $S_1$


$S_3$  is a 1-successor of  $S_1$

## **k-successors of a State**

**If we have two input signals, e.g.,  $w_0$  and  $w_1$ , then  $k$  can only be equal to 0, 1, 2, or 3.**
 
# k-successors of a State

If we have two input signals, e.g.,  $w_0$  and  $w_1$ , then  $k$  can only be equal to 0, 1, 2, or 3.



$S_1$  is a 3-successor of  $S_2$

$S_4$  is a 3-successor of  $S_2$

# Equivalence of states

“If states  $S_i$  and  $S_j$  are equivalent, then their corresponding  $k$ -successors (for all  $k$ ) are also equivalent.”

# Partition

**“A partition consists of one or more blocks, where each block comprises a subset of states that may be equivalent, but the states in a given block are definitely not equivalent to the states in other blocks.”**




# State Table for This Example

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

[ Figure 6.51 from the textbook ]


# State Diagram (just the states)

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

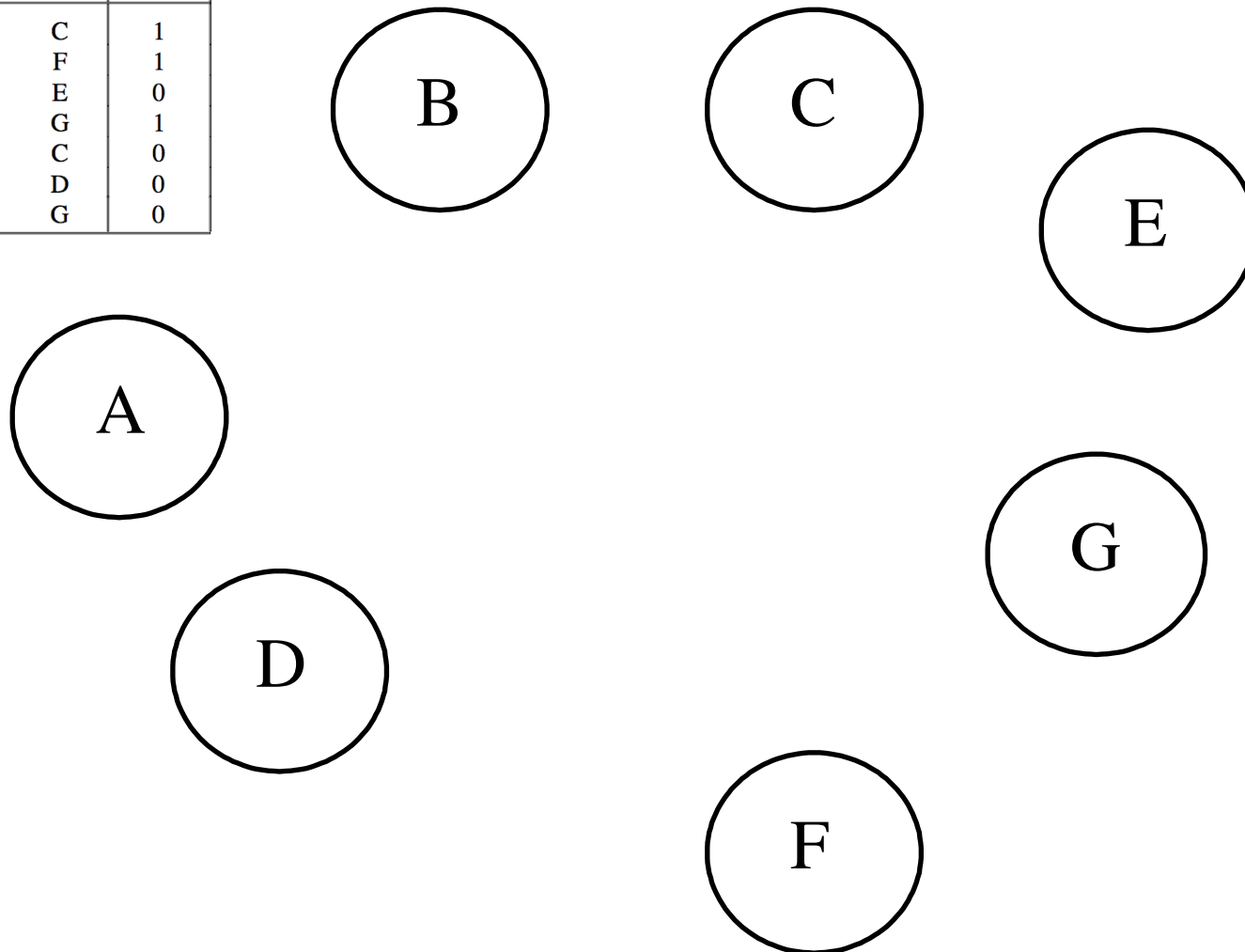


# State Diagram (transitions when $w=0$ )

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

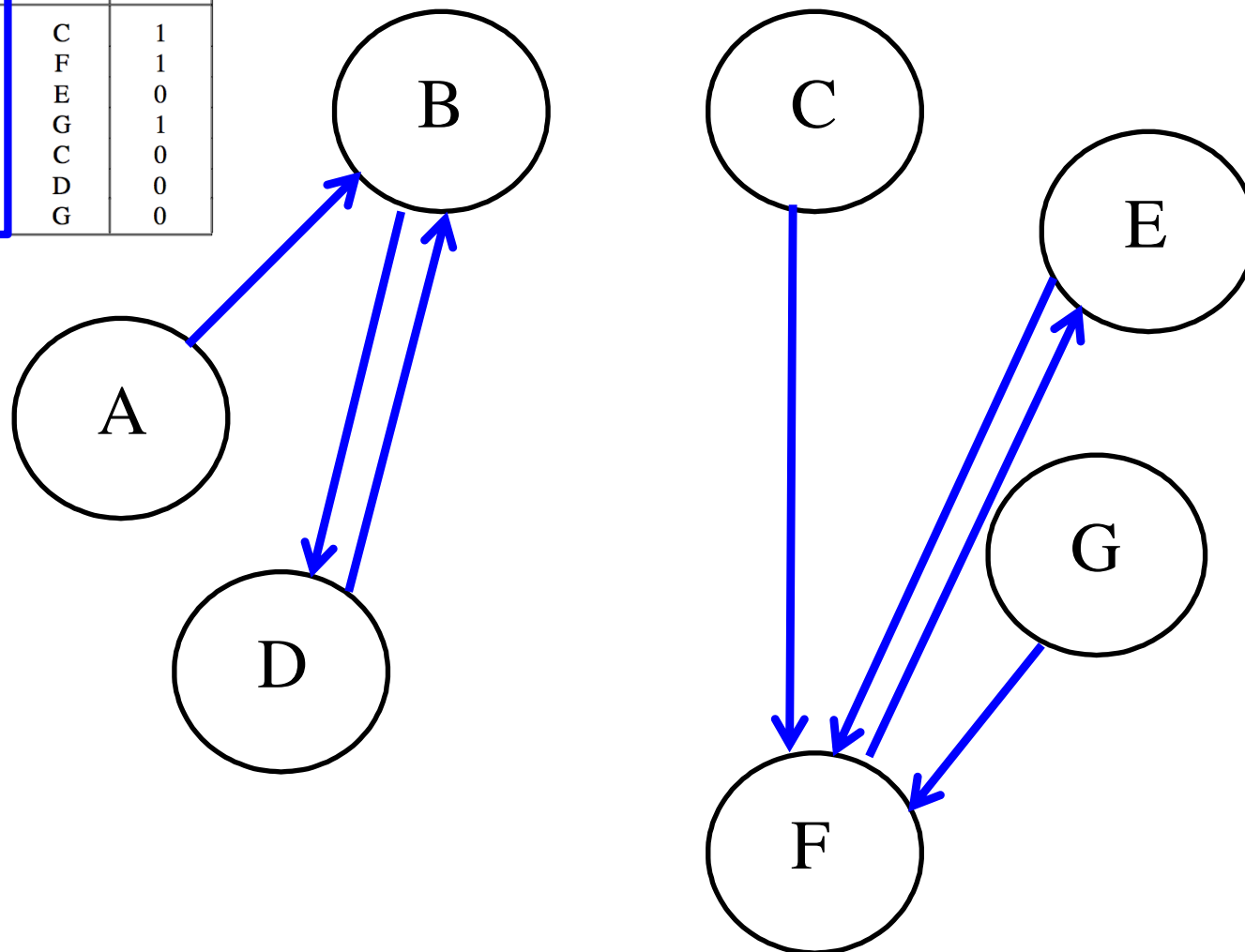


# State Diagram (transitions when $w=1$ )

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

 


# Outputs

Present state	Next state		Output
	$w = 0$	$w = 1$	$z$
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

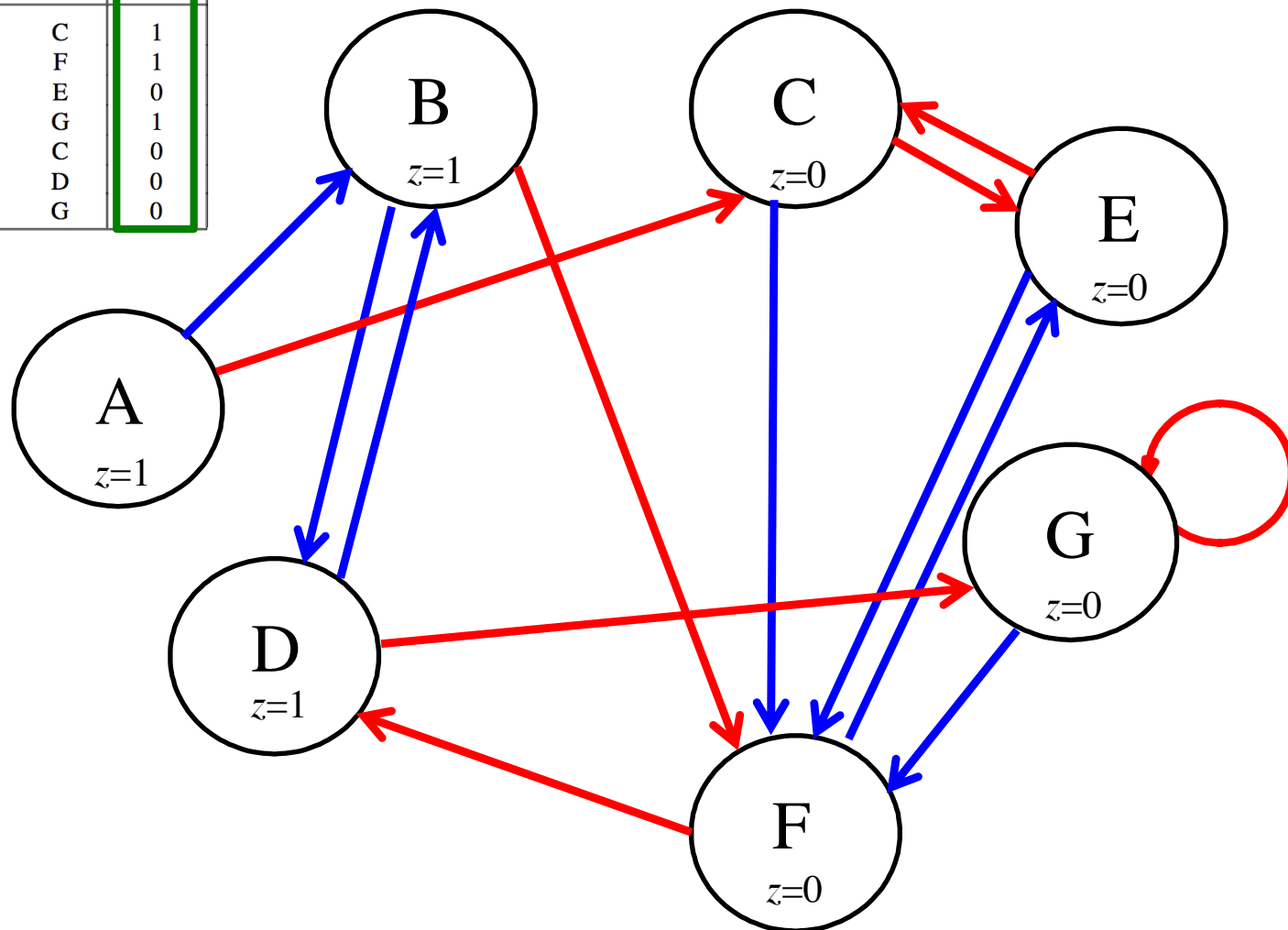


# Partition #1

(All states in the same partition)

 


# Partition #1

(ABCDEFGG)

 

## Partition #2


(based on outputs)

 




## Partition #2

(ABD)(CEFG)

 


# Partition #3.1

(Examine the 0-successors of ABD)

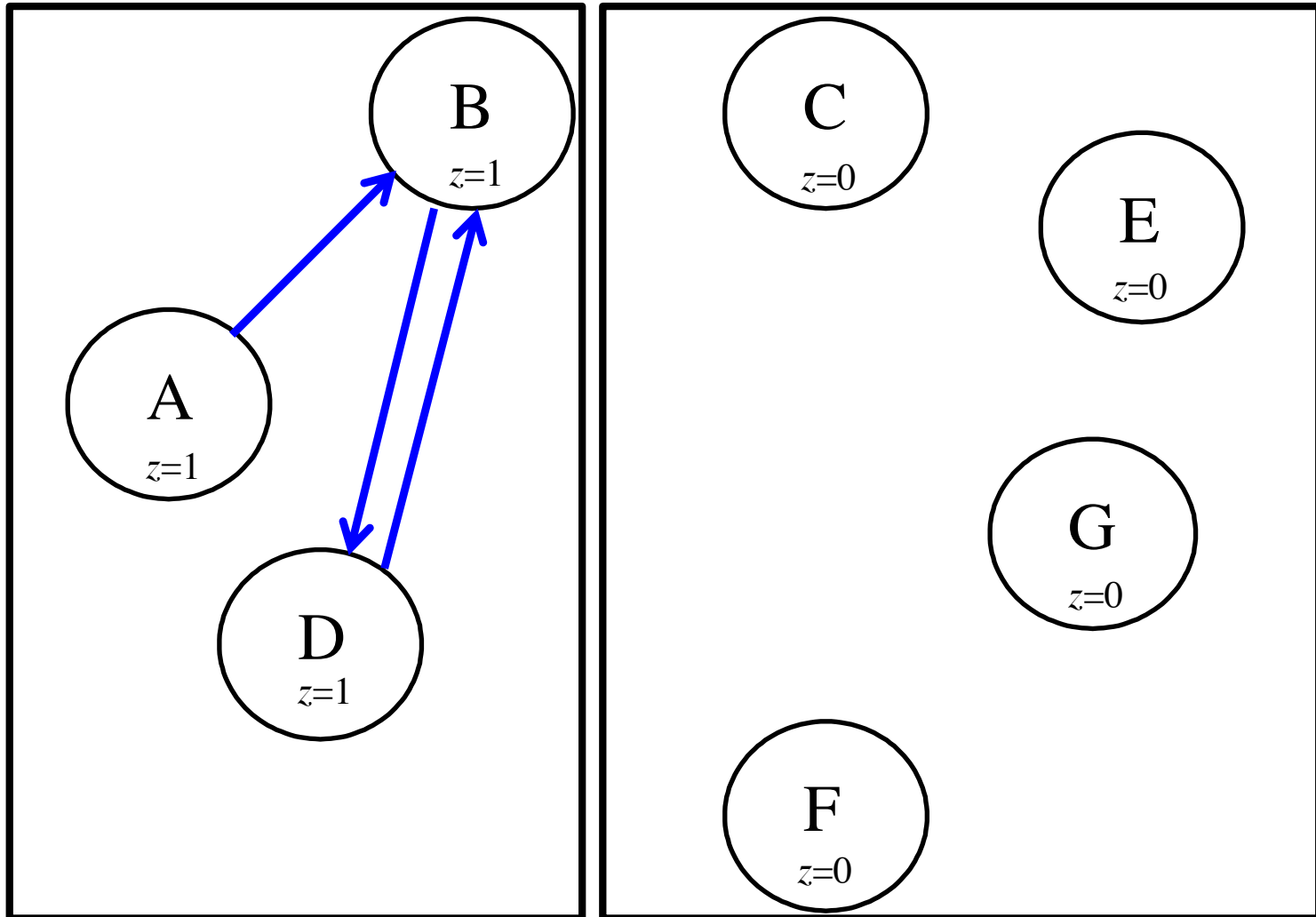


# Partition #3.1

(Examine the 1-successors of ABD)

 


## Partition #3.2

(Examine the 0-successors of C EFG)

 


## Partition #3.2

(Examine the 1-successors of C EFG)

 


## Partition #3.2

(Examine the 1-successors of CEF G)

 


# Partition #3

(ABD)(CEG)(F)

 

# Partition #3


(ABD)(CEG)(F)

 




# Partition #4.1

(Examine the 0-successors of ABD)

 

# Partition #4.1


(Examine the 1-successors of ABD)

 

# Partition #4.1


(Examine the 1-successors of ABD)

This needs to be  
in a new block

 


# Partition #4

(AD)(B)(CEG)(F)

 


# Partition #4

(AD)(B)(CEG)(F)

 


# Partition #5.1

(Examine the 0-successors of AD)

 


# Partition #5.1

(Examine the 1-successors of AD)

 

# Partition #5.2


(Examine the 0-successors of B)

 




# Partition #5.2

(Examine the 1-successors of B)

 


# Partition #5.3

(Examine the 0-successors of CEG)

 


# Partition #5.3

(Examine the 1-successors of CEG)

 


# Partition #5.4

(Examine the 0-successors of F)

 


# Partition #5.4

(Examine the 1-successors of F)

 


# Partition #5

(AD)(B)(CEG)(F)

 


# Partition #4

(AD)(B)(CEG)(F)

 

 
## Partition #5

(This is the same as #4 so we can stop here)







# Stop Here ...

 


... and Relabel All Partitions

 


... and Relabel All Partitions

 


# Merge the states in the same partition

 

 
**Merge the states in the same partition**




# Merge the states in the same partition

 

# Merge the states in the same partition

 


# Merge the states in the same partition

 





# Merge the states in the same partition

 


# Merge the states in the same partition

 


# Merge the states in the same partition

 

# Merge the transitions too

 

# The Minimized Graph

 

# Minimized state table


Present state	Nextstate		Output z
	w = 0	w = 1	
A	B	C	1
B	A	F	1
C	F	C	0
F	C	A	0

[ Figure 6.52 from the textbook ]

**To Summarize**

# Original State Diagram


Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

 




# Minimized State Diagram

Present state	Nextstate		Output z
	w = 0	w = 1	
A	B	C	1
B	A	F	1
C	F	C	0
F	C	A	0

 


# Minimized State Diagram

Present state	Nextstate		Output z
	w = 0	w = 1	
A	B	C	1
B	A	F	1
C	F	C	0
F	C	A	0

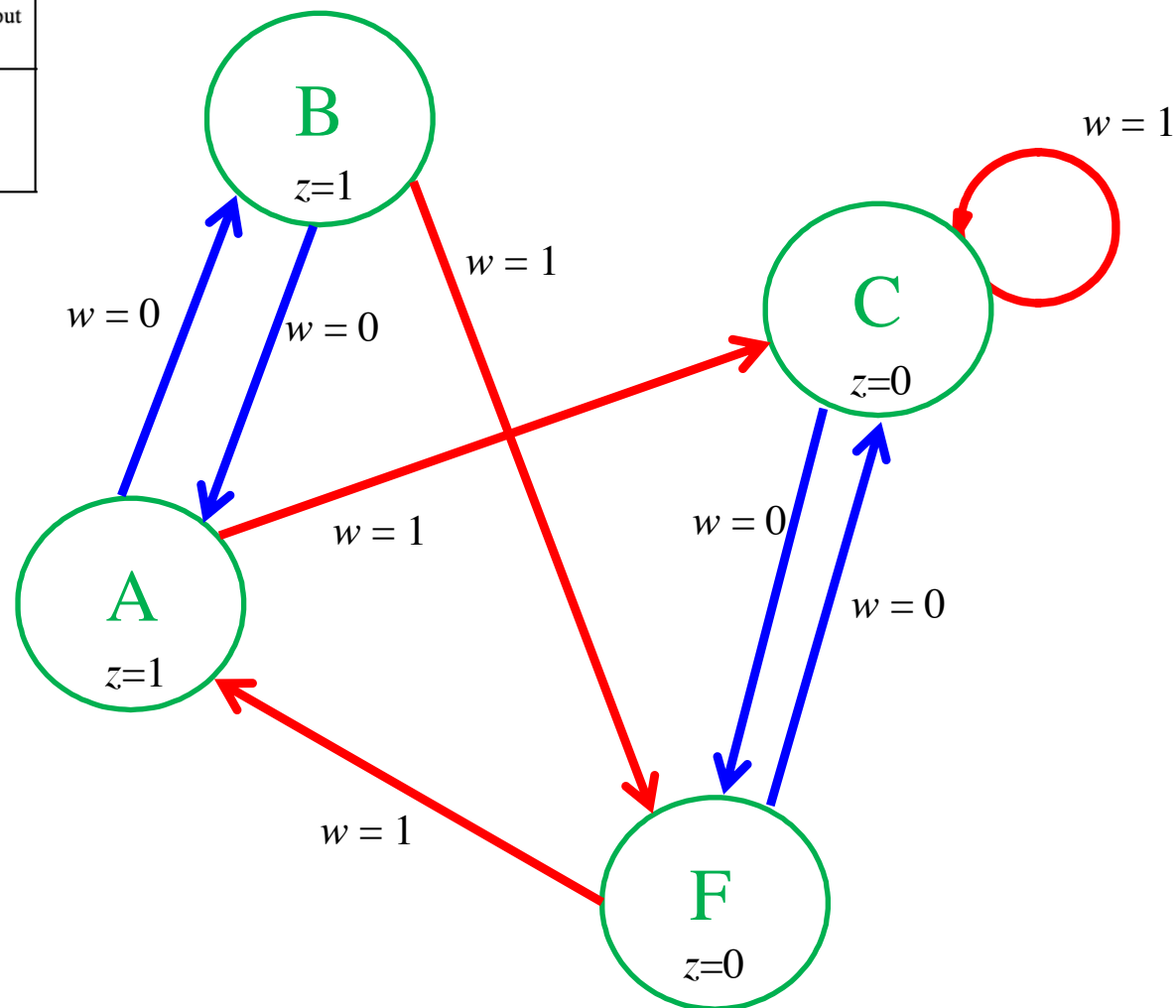

# Minimized State Diagram

Present state	Nextstate		Output z
	w = 0	w = 1	
A	B	C	1
B	A	F	1
C	F	C	0
F	C	A	0

 

# Minimized state table

Present state	Nextstate		Output z
	w = 0	w = 1	
A	B	C	1
B	A	F	1
C	F	C	0
F	C	A	0


[ Figure 6.52 from the textbook ]

# **Vending Machine Example (Moore-Type)**

# Vending Machine Example

- The machine accepts nickels and dimes
- It takes 15 cents for a piece of candy to be released from the machine
- If 20 cents is deposited, the machine will not return the change, but it will credit the buyer with 5 cents and wait for the buyer to make a second purchase.


# Signals for the vending machine

 

(a) Timing diagram

[ Figure 6.53.a from the textbook ]


# Signals for the vending machine

 

The nickel sensor will be ON  
for several clock cycles  
while the coin is falling down.




# Signals for the vending machine

 


But the FSM needs a nickel signal (N)  
that is ON for only one clock cycle.

# Signals for the vending machine

 


Similarly, for the dime sensor  
and the dime signal (D).

# Signals for the vending machine

 


(a) Timing diagram

 


(b) Circuit that generates *N*

[ Figure 6.53 from the textbook ]

# Signals for the vending machine

 


(a) Timing diagram

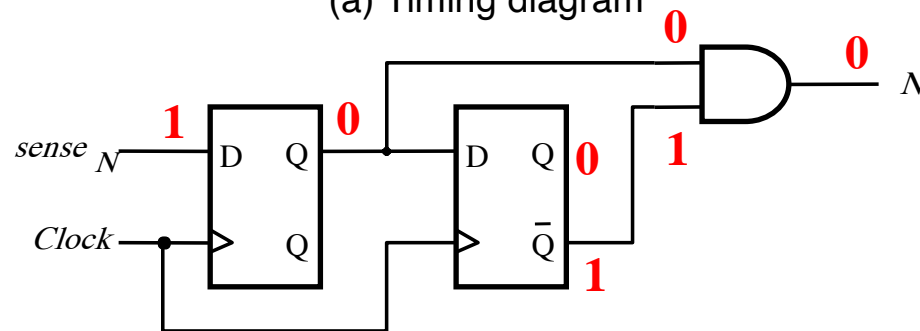


(b) Circuit that generates  $N$

[ Figure 6.53 from the textbook ]

# Signals for the vending machine

 


(a) Timing diagram

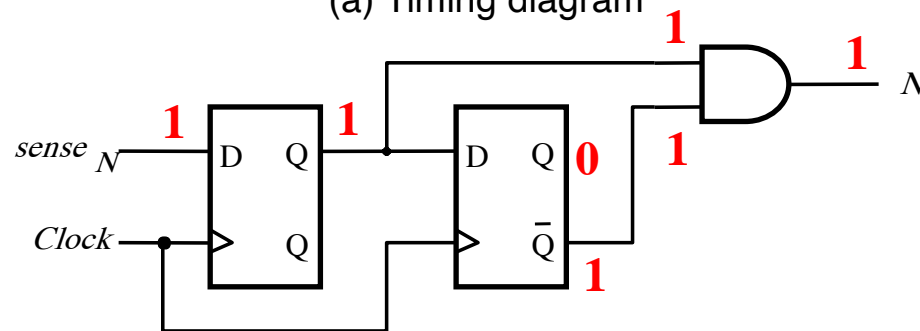


(b) Circuit that generates  $N$

[ Figure 6.53 from the textbook ]

# Signals for the vending machine

 


(a) Timing diagram

 


(b) Circuit that generates *N*

[ Figure 6.53 from the textbook ]

# Signals for the vending machine

 


(a) Timing diagram

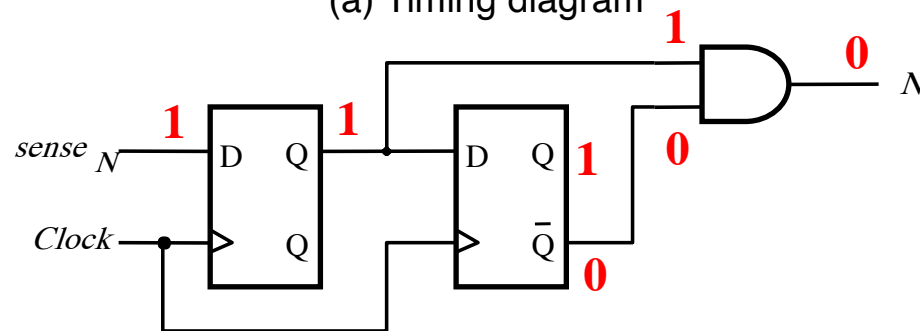


(b) Circuit that generates *N*

[ Figure 6.53 from the textbook ]

# Signals for the vending machine

 

(a) Timing diagram

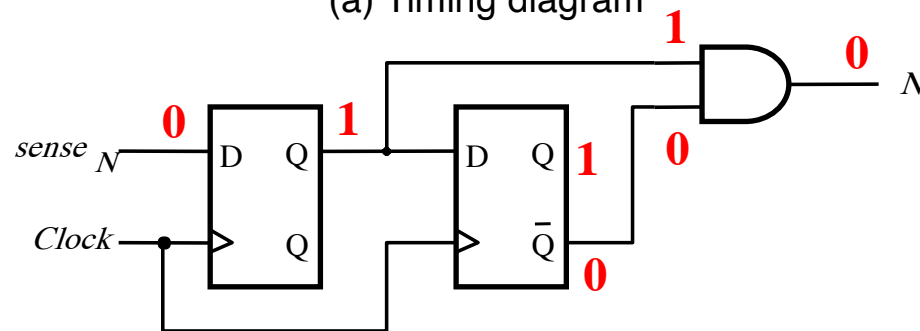


(b) Circuit that generates *N*


[ Figure 6.53 from the textbook ]



# Signals for the vending machine

 


(a) Timing diagram

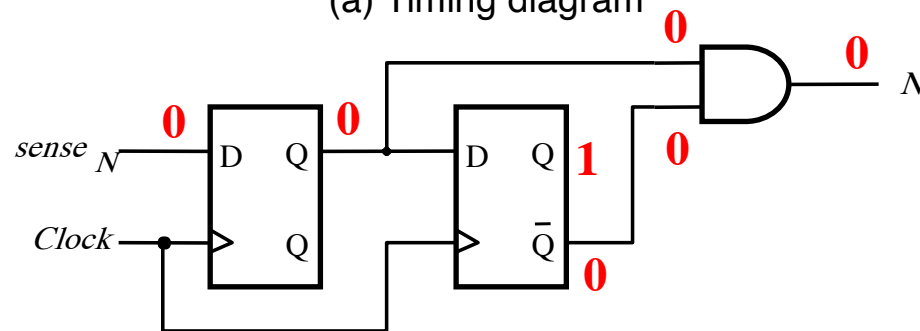


(b) Circuit that generates  $N$

[ Figure 6.53 from the textbook ]

# Signals for the vending machine

 


(a) Timing diagram

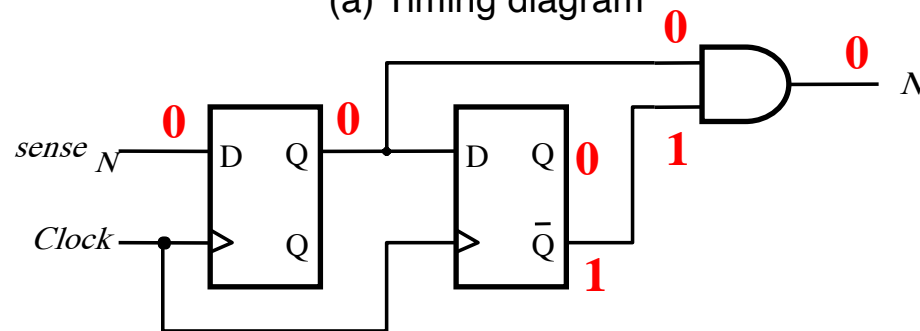

(b) Circuit that generates  $N$


[ Figure 6.53 from the textbook ]

# State Diagram for the vending machine

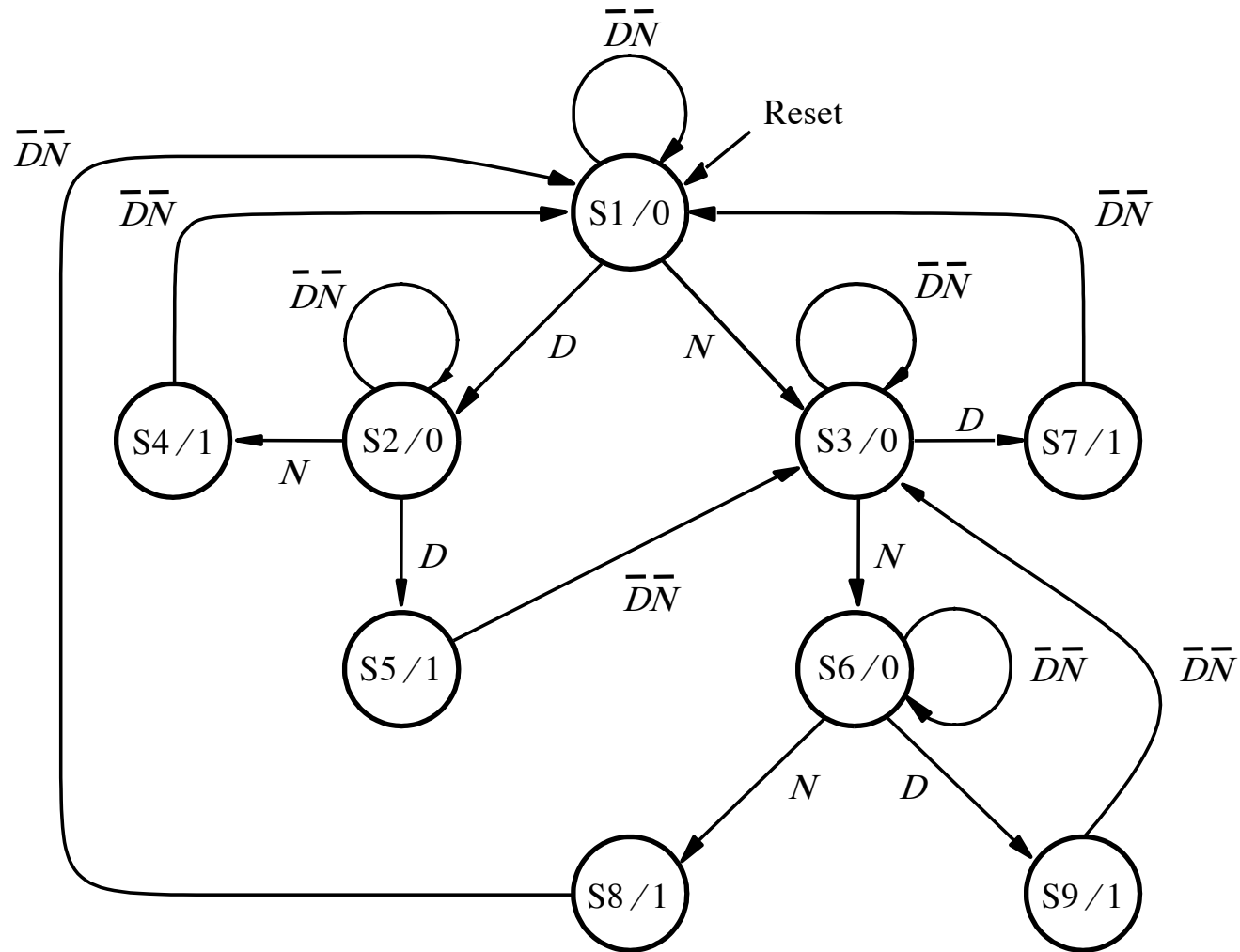

[ Figure 6.54 from the textbook ]

# State Diagram for the vending machine

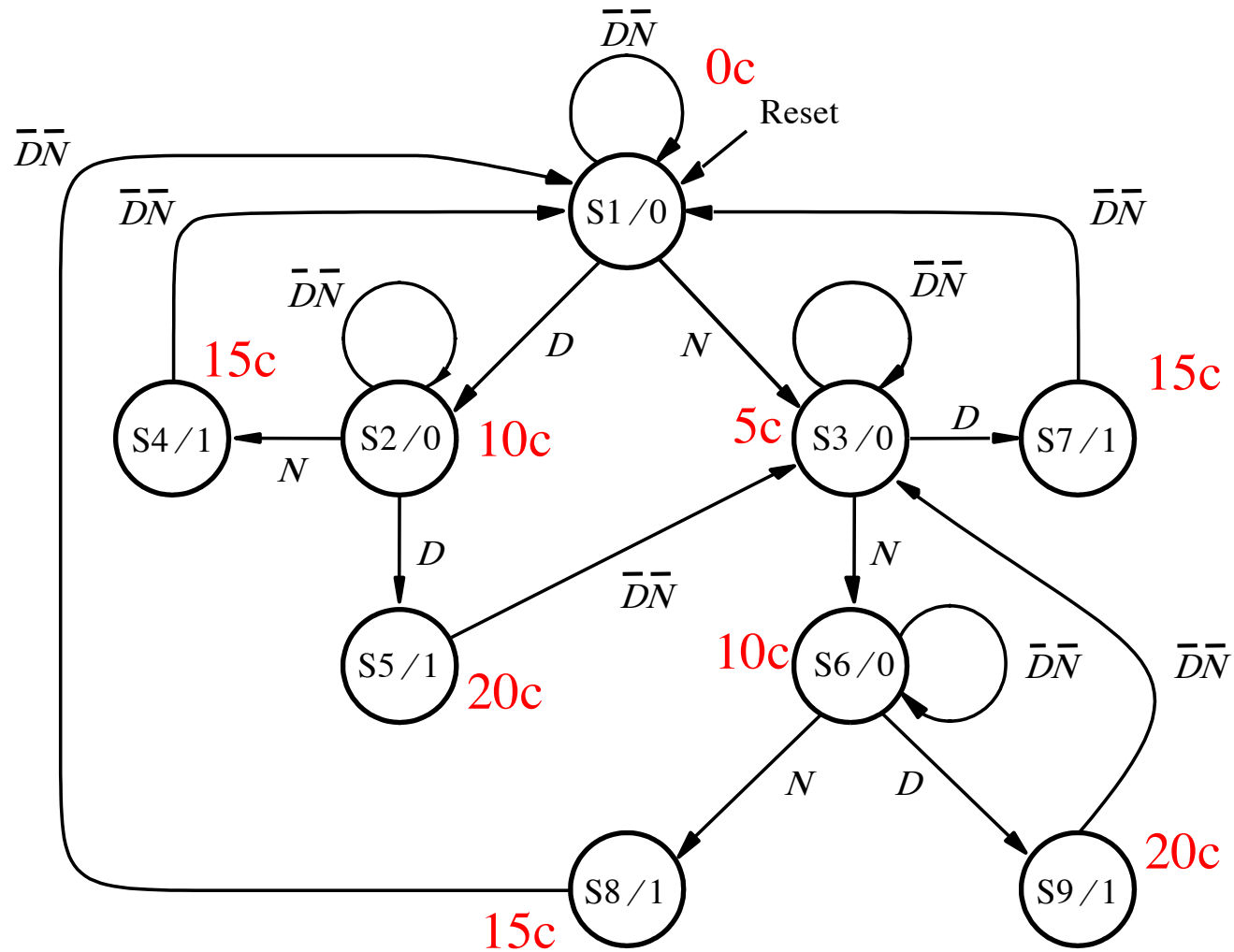

[ Figure 6.54 from the textbook ]

# State Table for the vending machine

Present state	Next state					Output $z$
	$DN$	$=00$	01	10	11	
S1	S1	S3	S2	—		0
S2	S2	S4	S5	—		0
S3	S3	S6	S7	—		0
S4	S1	—	—	—		1
S5	S3	—	—	—		1
S6	S6	S8	S9	—		0
S7	S1	—	—	—		1
S8	S1	—	—	—		1
S9	S3	—	—	—		1

Incompletely specified state table

# State Table for the vending machine

Present state	Next state				Output $z$
	$DN$	$=00$	$01$	$10$	$11$
S1	S1	S3	S2	—	0
S2	S2	S4	S5	—	0
S3	S3	S6	S7	—	0
S4	S1	—	—	—	1
S5	S3	—	—	—	1
S6	S6	S8	S9	—	0
S7	S1	—	—	—	1
S8	S1	—	—	—	1
S9	S3	—	—	—	1

Incompletely specified state table

We cannot insert both a nickel and a dime at the same time.

# State Table for the vending machine


Present state	Next state					Output $z$
	$DN$	$=00$	$01$	$10$	$11$	
S1	S1	S3	S2	—	—	0
S2	S2	S4	S5	—	—	0
S3	S3	S6	S7	—	—	0
S4	S1	—	—	—	—	1
S5	S3	—	—	—	—	1
S6	S6	S8	S9	—	—	0
S7	S1	—	—	—	—	1
S8	S1	—	—	—	—	1
S9	S3	—	—	—	—	1

Incompletely specified state table

The machine is in S4 and S5 for only 1 clock cycle.

Which is shorter than the time it takes for the coin to fall down. It is physically impossible for another coin to be inserted at that time.

# State Diagram for the vending machine

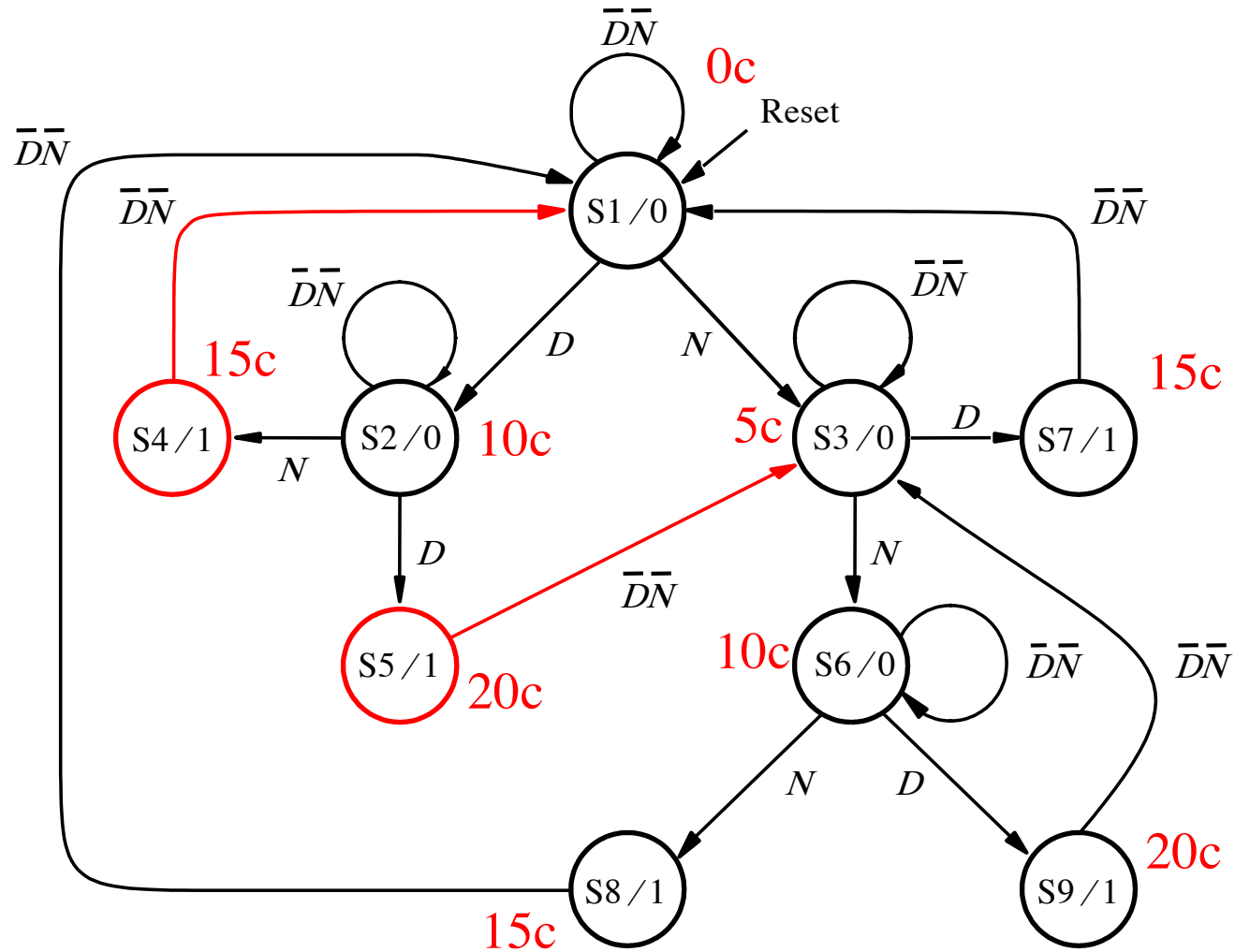

[ Figure 6.54 from the textbook ]




# State Table for the vending machine

Present state	Next state					Output $z$
	$DN$	$=00$	$01$	$10$	$11$	
S1	S1	S3	S2	—		0
S2	S2	S4	S5	—		0
S3	S3	S6	S7	—		0
S4	S1	—	—	—		1
S5	S3	—	—	—		1
S6	S6	S8	S9	—		0
S7	S1	—	—	—		1
S8	S1	—	—	—		1
S9	S3	—	—	—		1

Incompletely specified state table

The machine is in states S7, S8, and S9 for only 1 clock cycle. Which is shorter than the time it takes for the coin to fall down.

# State Diagram for the vending machine

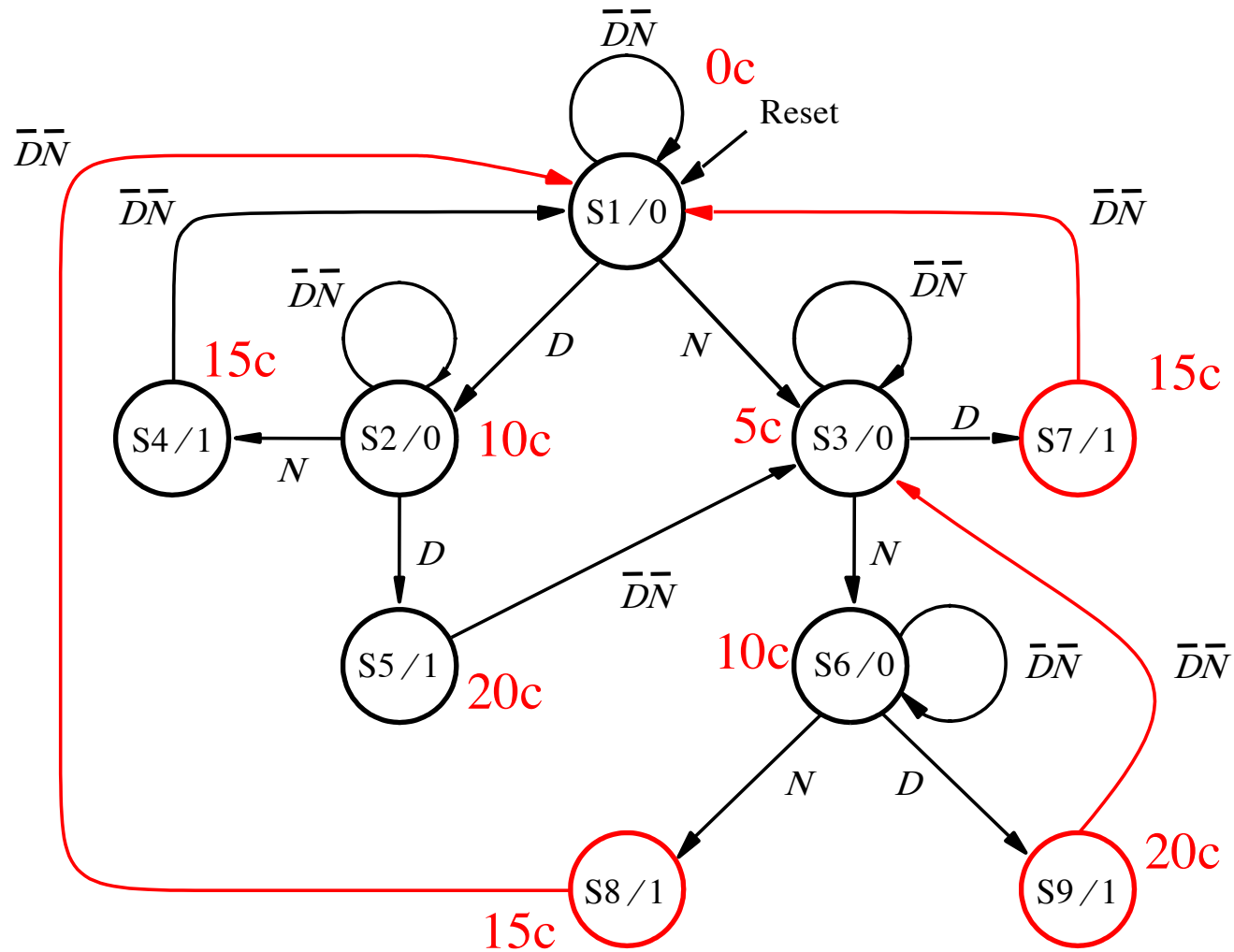

[ Figure 6.54 from the textbook ]

# Partition for Vending Machine FSM

Present state	Next state				Output
	00	01	10	11	z
S1	S1	S3	S2	-	0
S3	S3	S6	S7	-	0
S2	S2	S4	S5	-	0
S6	S6	S8	S9	-	0
S4	S1	-	-	-	1
S7	S1	-	-	-	1
S8	S1	-	-	-	1
S5	S3	-	-	-	1
S9	S3	-	-	-	1

$P1=(S1,S2,S3,S4,S5,S6,S7,S8,S9)$

# Partition for Vending Machine FSM

Present state	Next state				Output
	00	01	10	11	z
S1	S1	S3	S2	-	0
S3	S3	S6	S7	-	0
S2	S2	S4	S5	-	0
S6	S6	S8	S9	-	0
S4	S1	-	-	-	1
S7	S1	-	-	-	1
S8	S1	-	-	-	1
S5	S3	-	-	-	1
S9	S3	-	-	-	1

P1=(S1,S2,S3,S4,S5,S6,S7,S8,S9)

P2=(S1,S2,S3,S6) (S4,S5,S7,S8,S9)

partition based on  
common output

# Partition for Vending Machine FSM

Present state	Next state				Output
	00	01	10	11	z
S1	S1	S3	S2	-	0
S3	S3	S6	S7	-	0
S2	S2	S4	S5	-	0
S6	S6	S8	S9	-	0
S4	S1	-	-	-	1
S7	S1	-	-	-	1
S8	S1	-	-	-	1
S5	S3	-	-	-	1
S9	S3	-	-	-	1

P1=(S1,S2,S3,S4,S5,S6,S7,S8,S9)

P2=(S1,S2,S3,S6) (S4,S5,S7,S8,S9)

P3=(S1) (S3) (S2,S6) (S4,S5,S7,S8,S9)

# Partition for Vending Machine FSM

Present state	Next state				Output
	00	01	10	11	z
S1	S1	S3	S2	-	0
S3	S3	S6	S7	-	0
S2	S2	S4	S5	-	0
S6	S6	S8	S9	-	0
S4	S1	-	-	-	1
S7	S1	-	-	-	1
S8	S1	-	-	-	1
S5	S3	-	-	-	1
S9	S3	-	-	-	1

P1=(S1,S2,S3,S4,S5,S6,S7,S8,S9)

P2=(S1,S2,S3,S6) (S4,S5,S7,S8,S9)

P3=(S1) (S3) (S2,S6) (S4,S5,S7,S8,S9)

P4=(S1) (S3) (S2,S6) (S4,S7,S8) (S5,S9)

# Partition for Vending Machine FSM

Present state	Next state				Output
	00	01	10	11	z
S1	S1	S3	S2	-	0
S3	S3	S6	S7	-	0
S2	S2	S4	S5	-	0
S6	S6	S8	S9	-	0
S4	S1	-	-	-	1
S7	S1	-	-	-	1
S8	S1	-	-	-	1
S5	S3	-	-	-	1
S9	S3	-	-	-	1

P1=(S1,S2,S3,S4,S5,S6,S7,S8,S9)

P2=(S1,S2,S3,S6) (S4,S5,S7,S8,S9)

P3=(S1) (S3) (S2,S6) (S4,S5,S7,S8,S9)

P4=(S1) (S3) (S2,S6) (S4,S7,S8) (S5,S9)

P5=(S1) (S3) (S2,S6) (S4,S7,S8) (S5,S9)

# Partition for Vending Machine FSM

Present state	Next state				Output
	00	01	10	11	z
S1	S1	S3	S2	-	0
S3	S3	S6	S7	-	0
S2	S2	S4	S5	-	0
S6	S6	S8	S9	-	0
S4	S1	-	-	-	1
S7	S1	-	-	-	1
S8	S1	-	-	-	1
S5	S3	-	-	-	1
S9	S3	-	-	-	1

P1=(S1,S2,S3,S4,S5,S6,S7,S8,S9)

P2=(S1,S2,S3,S6) (S4,S5,S7,S8,S9)

P3=(S1) (S3) (S2,S6) (S4,S5,S7,S8,S9)

P4=(S1) (S3) (S2,S6) (S4,S7,S8) (S5,S9)

P5=(S1) (S3) (S2,S6) (S4,S7,S8) (S5,S9)




# Minimized State Table for the vending machine

Present state	Next state					Output $z$
	$DN$	$=00$	$01$	$10$	$11$	
S1	S1	S3	S2	—	0	
S2	S2	S4	S5	—	0	
S3	S3	S2	S4	—	0	
S4	S1	—	—	—	1	
S5	S3	—	—	—	1	

[ Figure 6.56 from the textbook ]

# Minimized State Table for the vending machine

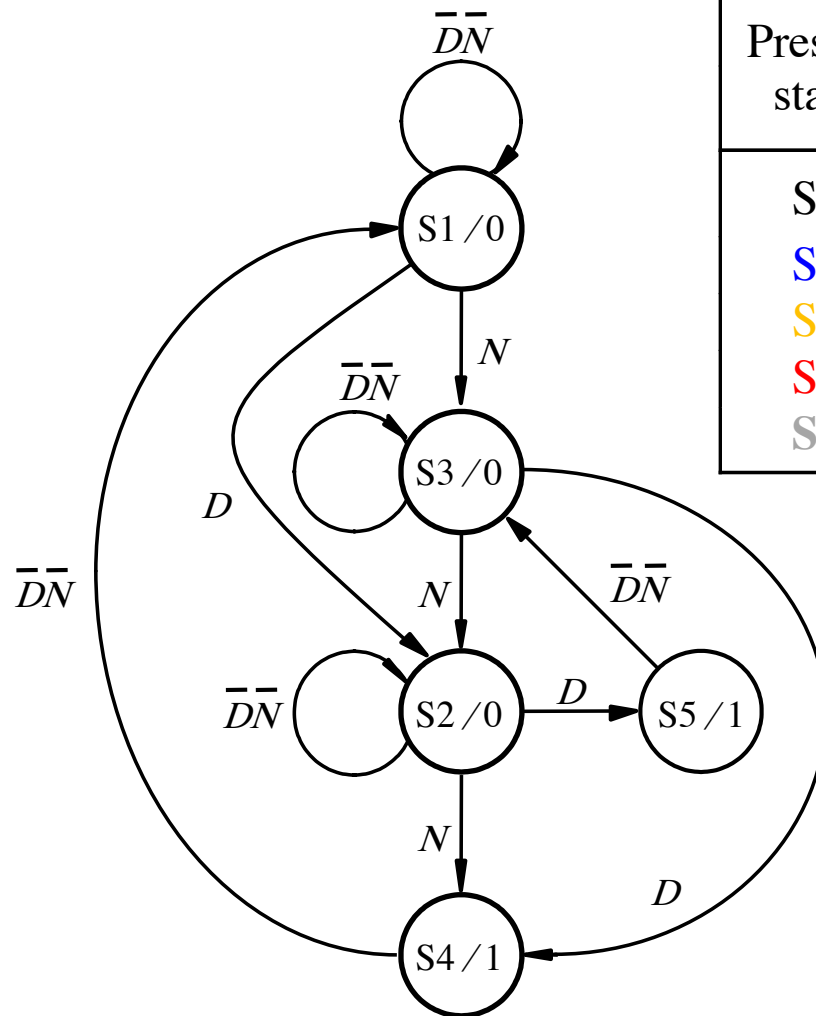


[ Figure 6.57 from the textbook ]

Present state	Next state				Output $z$
	$DN$	$=00$	$01$	$10$	$11$
S1	S1	S3	S2	—	0
S2	S2	S4	S5	—	0
S3	S3	S2	S4	—	0
S4	S1	—	—	—	1
S5	S3	—	—	—	1


[ Figure 6.56 from the textbook ]

# Minimized State Diagram for the vending machine

 

[ Figure 6.57 from the textbook ]


# Minimized State Diagram for the vending machine

 

[ Figure 6.57 from the textbook ]


# **Vending Machine Example (Mealy-Type)**

## Mealy-type FSM for the vending machine

 

[ Figure 6.58 from the textbook ]

# Mealy-type FSM for the vending machine

 

[ Figure 6.58 from the textbook ]





## Another Example of Incompletely specified state table

Present state	Next state		Output $z$	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

[ Figure 6.59 from the textbook ]

**Questions?**

**THE END**