Module B4

Problem 1

Consider the power system shown below. Choose a system power base 100MVA and a line-to-line voltage base for section 1 as 6.9kV. The load in section 3 consumes 10MVA at 0.8pf leading when the line-to-line voltage at the load is 13.8kV

- (a) Determine the ohmic value of a R+jX load (R and X connected in series, as shown) in section 3 that consumes this same amount of power at the specified voltage level (i.e., that consumes 10 MVA at 0.8 pf leading at 13.8kV line-to-line).
- (b) Compute the impedance base for the section 3 load.



Solution to problem 1

(a)
$$S = \frac{V_{LL}^2}{Z^*} \Rightarrow Z = \frac{V_{LL}^2}{S^*} = \frac{(13.8 \times 10^3)^2}{10 \times 10^6 (0.8 + j0.6)} = \frac{15.235 - j11.426\Omega}{10 \times 10^6 (0.8 + j0.6)}$$

(b) $V_{BASE} = 6.9 \left[\frac{6.9}{6.8} \right] = 70.015$
 $V_{BASE} = 70.015 \left[\frac{13.8}{71} \right] = 13.608$
 $Z_{BASE} = \frac{\left(V_{BASE}\right)^2}{S_{BASE}} = \frac{\left(13.608 \times 10^3\right)^2}{S_{BASE}} = 1.8519 \Omega$

Problem 2

Consider the power system shown below. Choose a system power base of 100MVA and a line-to-line voltage base for section 1 as 6.9kV. Determine the appropriate values of per unit impedance for transformers T1, T2, ad the transmission line.



Solution to problem 2

$$\begin{aligned} V_{base,2} &= 6.9 \cdot \left(\frac{69}{6.8}\right) = 70.015, \quad V_{base,3} = 70.015 \cdot \left(\frac{13.8}{71}\right) = 13.61 \, p.u. \\ X_{T1,new} &= 0.10 \cdot \left(\frac{6.8}{6.9}\right)^2 \cdot \left(\frac{100}{50}\right) = \underline{0.1942} \\ X_{T2,new} &= 0.08 \cdot \left(\frac{71}{70.015}\right)^2 \cdot \left(\frac{100}{20}\right) = 0.08 \cdot \left(\frac{13.8}{13.61}\right)^2 \cdot \left(\frac{100}{20}\right) = \underline{0.4112} \\ Z_{base,2} &= \frac{\left(70.015 \times 10^3\right)^2}{100 \times 10^6} = 49.021\Omega \quad \Rightarrow X_L = \frac{5 + j20}{49.021} = \underline{0.102 + j0.4081} \end{aligned}$$

Problem 3

A generator is connected to a transmission line through a transformer having a rated turns ratio (ratio of line to line voltages) of:

20 kV (generator side) to 100 kV (transmission line side).

The generator has a per unit reactance of 0.08 pu on a 19 kV, 50 MVA base.

Select the base voltage on the transmission line side to be 110 kV.

- a. Compute the base voltage on the generator side.
- b. Compute the pu reactance of the generator using a 100 MVA system power base.

Solution to problem 3

(a)

$$V_{basegen} = 110kV \cdot \left[\frac{20kV}{100kV}\right] = 22kV$$

(b)

$$X_{pu2} = X_{pu1} \cdot \left[\frac{V_{basel}}{V_{base2}}\right]^2 \cdot \left[\frac{S_{base2}}{S_{base1}}\right] = 0.08 \cdot \left[\frac{19kV}{22kV}\right]^2 \cdot \left[\frac{100MVA}{50MVA}\right] = 0.11934$$

Problem 4

Choose a system MVA base of 100 MVA and a voltage base of 4.0 kV for the load portion of the system. Find per-unit values of impedances for both transformers and the transmission line.



Solution to problem 4

$$\begin{aligned} V_{base2} &= (4.0kV) \cdot \left(\frac{36kV}{4.5kV}\right) = 32kV \\ V_{base2} &= (32kV) \cdot \left(\frac{4.1kV}{34.5kV}\right) = 3.803kV \\ T1: X_{T1} &= X_{puT1} \cdot \left[\frac{V_{baseold}}{V_{basenew}}\right]^2 \cdot \left[\frac{S_{basenew}}{S_{baseold}}\right] = 0.10 \cdot \left[\frac{4.1kV}{3.803kV}\right]^2 \cdot \left[\frac{100MVA}{15MVA}\right] = 0.7749 \\ T2: X_{T2} &= X_{puT2} \cdot \left[\frac{V_{baseold}}{V_{basenew}}\right]^2 \cdot \left[\frac{S_{basenew}}{S_{baseold}}\right] = 0.08 \cdot \left[\frac{4.5kV}{4.0kV}\right]^2 \cdot \left[\frac{100MVA}{20MVA}\right] = 0.506 \\ Line: Z_{base} &= \frac{(32kV)^2}{100MVA} = 10.24\Omega \Rightarrow Z_{pu} = \frac{6\Omega}{10.24\Omega} = 0.586 \end{aligned}$$

Problem 5

- 1. B4: You receive the following data from a manufacturer regarding a new three phase transformer:
 - Ratio of line-line voltages:13.8kV/225kVPower rating:400 MVAPer unit reactance on component base:8%

You are considering replacement of an existing transformer in your three-phase system with this new one, and you want to see how it would affect the currents. Below is a circuit of your system. All data is in per unit on a 100 MVA base. The voltage base for the transmission line is 230 kV and the voltage base for the low side of transformer 1 is 14.1067 kV. The per unit impedances of the transmission line, transformer 2, and the load are:

 $Z_t\!\!=\!\!0.0004\!+\!j0.005 \hspace{0.1cm} \text{pu} \hspace{0.1cm} X_{X2}\!\!=\!\!0.02 \hspace{0.1cm} \text{pu} \hspace{0.1cm} R_L\!\!=\!\!0.8 \hspace{0.1cm} \text{pu}$

- a. Compute the per unit reactance of the transformer on the system bases.
- b. Compute the magnitude of the current I_t in the transmission line, in per unit, and in amperes.



Solution to problem 5

a. b. $X_{x1} = 0.08 \left(\frac{225}{230}\right)^2 \left(\frac{100}{400}\right) = 0.0191 \,\mathrm{pu}$

$$I_{t,pu} = \frac{1.0}{X_{x1} + Z_t + X_{x2} + R_L} = \frac{1.0}{j0.0191 + 0.0004 + j0.005 + j0.02 + 0.8} = \frac{1.0}{0.8004 + j0.0441} = 1.2456 - j0.0686$$

And the current magnitude, in per unit, is given by $|I_t| = \sqrt{[(1.2456)^2 + (0.0686)^2]} = 1.2475$ pu To get amperes, we need the current base for the transmission line section of the system. This is:

$$I_{base} = \frac{100 \times 10^6}{\sqrt{3}(230 \times 10^3)} = 251 \implies I_t = 1.2475(251) = 313.1 \text{ amperes}$$