


Module B3

Three Phase Analysis

B3.2

Balanced Three Phase Circuits

Delta Connection

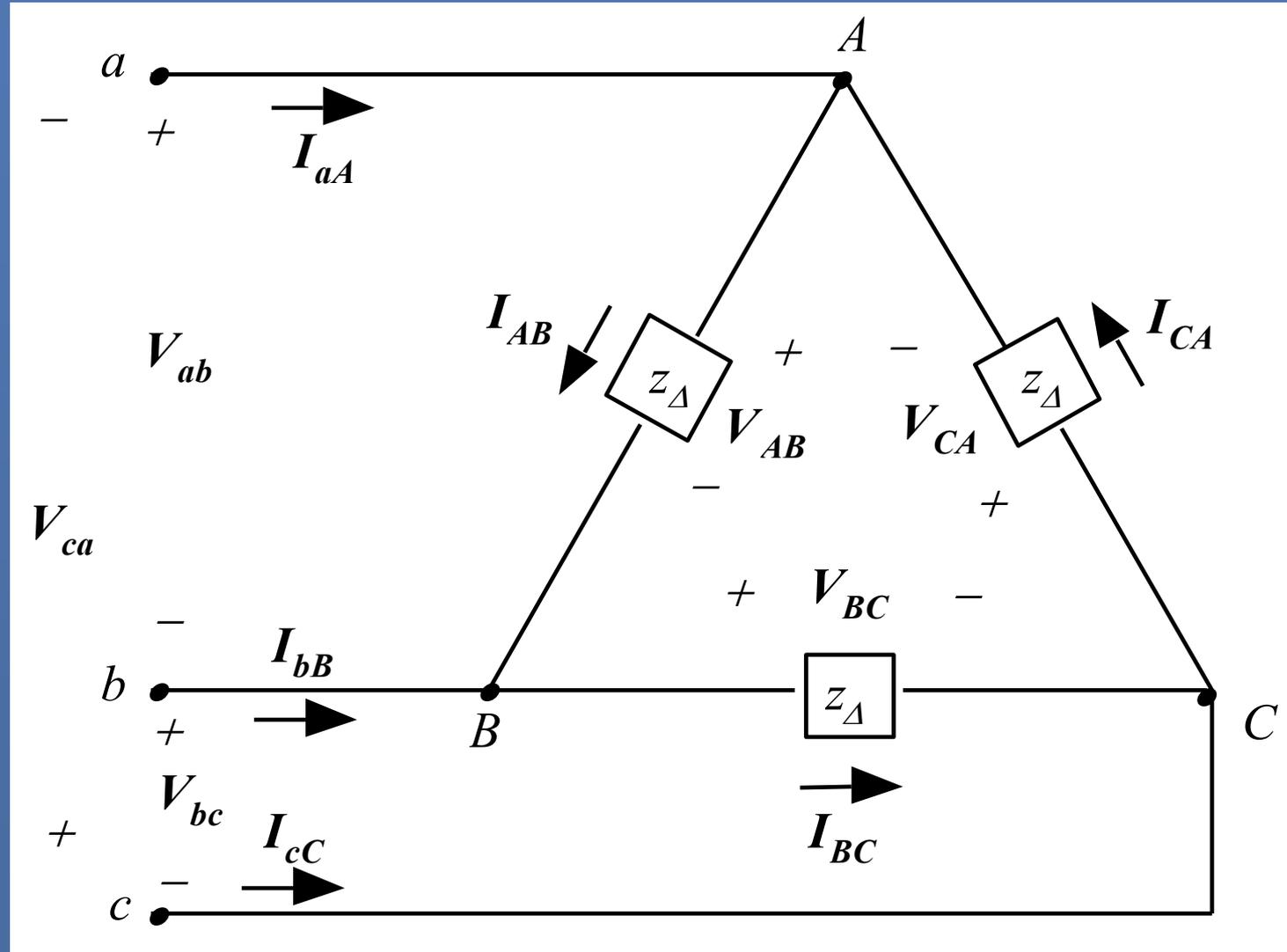

$$V_{AB} = V_{\phi}$$

$$I_{AB} = I_{\phi} \angle 0^{\circ}$$

$$I_{BC} = I_{\phi} \angle -120^{\circ}$$

$$I_{CA} = I_{\phi} \angle +120^{\circ}$$

$$I_{aA} = I_{AB} - I_{CA} = I_{\phi} \angle 0^{\circ} - I_{\phi} \angle 120^{\circ} = \sqrt{3} I_{\phi} \angle -30^{\circ}$$

$$I_{bB} = I_{BC} - I_{AB} = I_{\phi} \angle -120^{\circ} - I_{\phi} \angle 0^{\circ} = \sqrt{3} I_{\phi} \angle -150^{\circ}$$

$$I_{cC} = I_{CA} - I_{BC} = I_{\phi} \angle 120^{\circ} - I_{\phi} \angle -120^{\circ} = \sqrt{3} I_{\phi} \angle 90^{\circ}$$


Delta connection:

Line-line voltages equal phase voltages

Line currents are $\sqrt{3}$ times
phase currents in magnitude
and lag them by 30 degrees in angle.

Delta: Line Currents Lag: Delta-LC-LAG

WYE Connection

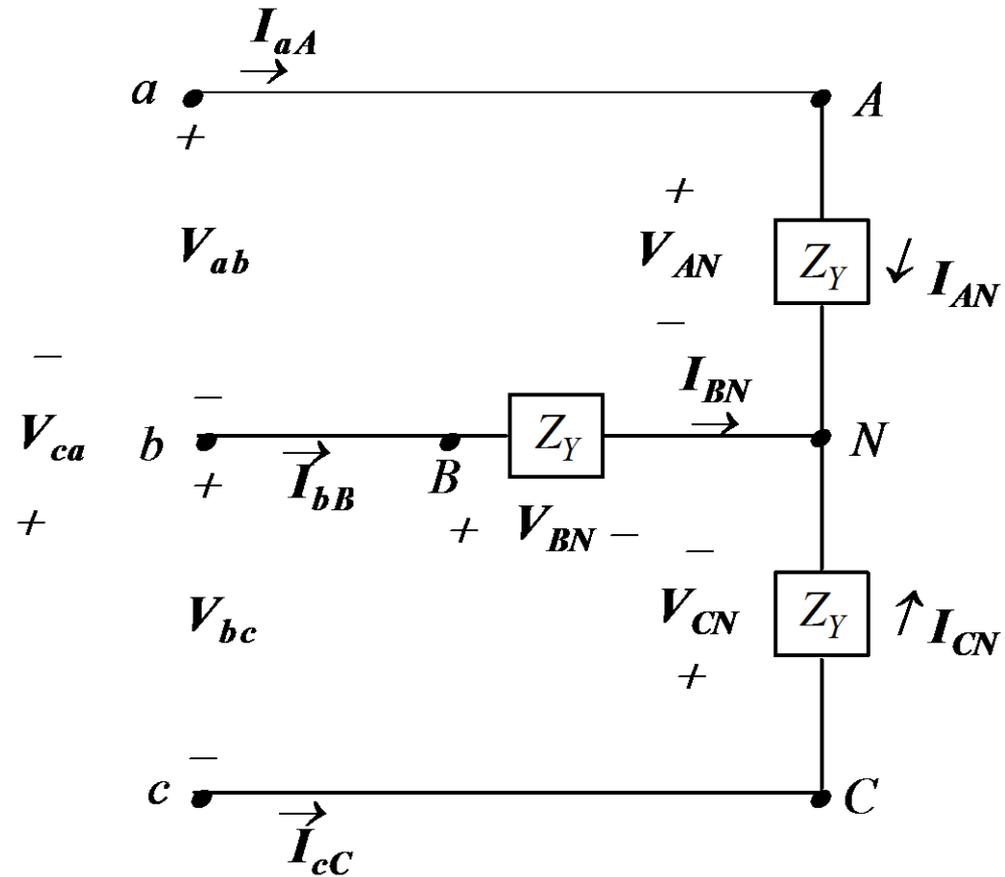

I_{aA} is equal to the phase current $I_{AN} = I_{\phi}$

$$V_{AN} = V_{\phi} \angle 0^{\circ}$$

$$V_{BN} = V_{\phi} \angle -120^{\circ}$$

$$V_{CN} = V_{\phi} \angle +120^{\circ}$$

$$V_{AB} = V_{AN} - V_{BN} = V_{\phi} - V_{\phi} \angle -120^{\circ} = \sqrt{3} V_{\phi} \angle 30^{\circ}$$

$$V_{BC} = V_{BN} - V_{CN} = V_{\phi} \angle -120^{\circ} - V_{\phi} \angle 120^{\circ} = \sqrt{3} V_{\phi} \angle -90^{\circ}$$

$$V_{CA} = V_{CN} - V_{AN} = V_{\phi} \angle 120^{\circ} - V_{\phi} \angle 0^{\circ} = \sqrt{3} V_{\phi} \angle 150^{\circ}$$

Wye connection:

Line-Line voltages are $\sqrt{3}$ times phase voltages in magnitude and lead them by 30 degrees in angle.

Y: Line-Line Voltages Lead: Y-LV-Lead-

Line currents equal phase currents

Power relations for three phase circuits

$$P = 3V_{\phi} I_{\phi} \cos \theta$$

$$P = \sqrt{3} V_L I_L \cos \theta$$

$$Q = 3V_{\phi} I_{\phi} \sin \theta$$

$$Q = \sqrt{3} V_L I_L \sin \theta$$

$$S = P + jQ$$

$$|S| = \sqrt{P^2 + Q^2} = \sqrt{3} V_L I_L$$

- can be used for Wye or Delta
- all quantities are magnitudes
- θ is the angle for which \mathbf{V}_{ϕ} leads \mathbf{I}_{ϕ}
- Positive Q is for power flowing into L load
- Negative Q is for power flowing “into” C load

Per-phase analysis of 3 phase circuits

- Convert all delta connections to Y connections using

$$Z_Y = \frac{Z_{\Delta}}{3}$$

- “Lift out” the a-phase to neutral circuit
- Perform single phase analysis using phase quantities and per phase powers
- Multiply all powers by 3 to get solution in terms of three phase powers.

Example B3.2

Three balanced three-phase loads are connected in parallel. Load 1 is Y-connected with an impedance of $150 + j50$; load 2 is delta-connected with an impedance of $900 + j600$; and load 3 is 95.04 kVA at 0.6 pf leading. The loads are fed from a distribution line with an impedance of $3 + j24$. The magnitude of the line-to-neutral voltage at the load end of the line is 4.8 kV.

- a) Calculate the total complex power at the sending end of the line.
- b) What percent of the average power at the sending end of the line is delivered to the load?

Solution:

Load 1: $Z_1 = 150 + j50$


Load 2: $Z_2 = (900 + j600)/3 = 300 + j200$

Load 3:

$$S_{3/\phi} = \frac{95040}{3} (0.6 - j0.8)$$
$$= 19,008 - j25,344 \text{ VA}$$

$$V_{\phi} = 4800 \text{ volts}$$

Per phase equivalent circuit

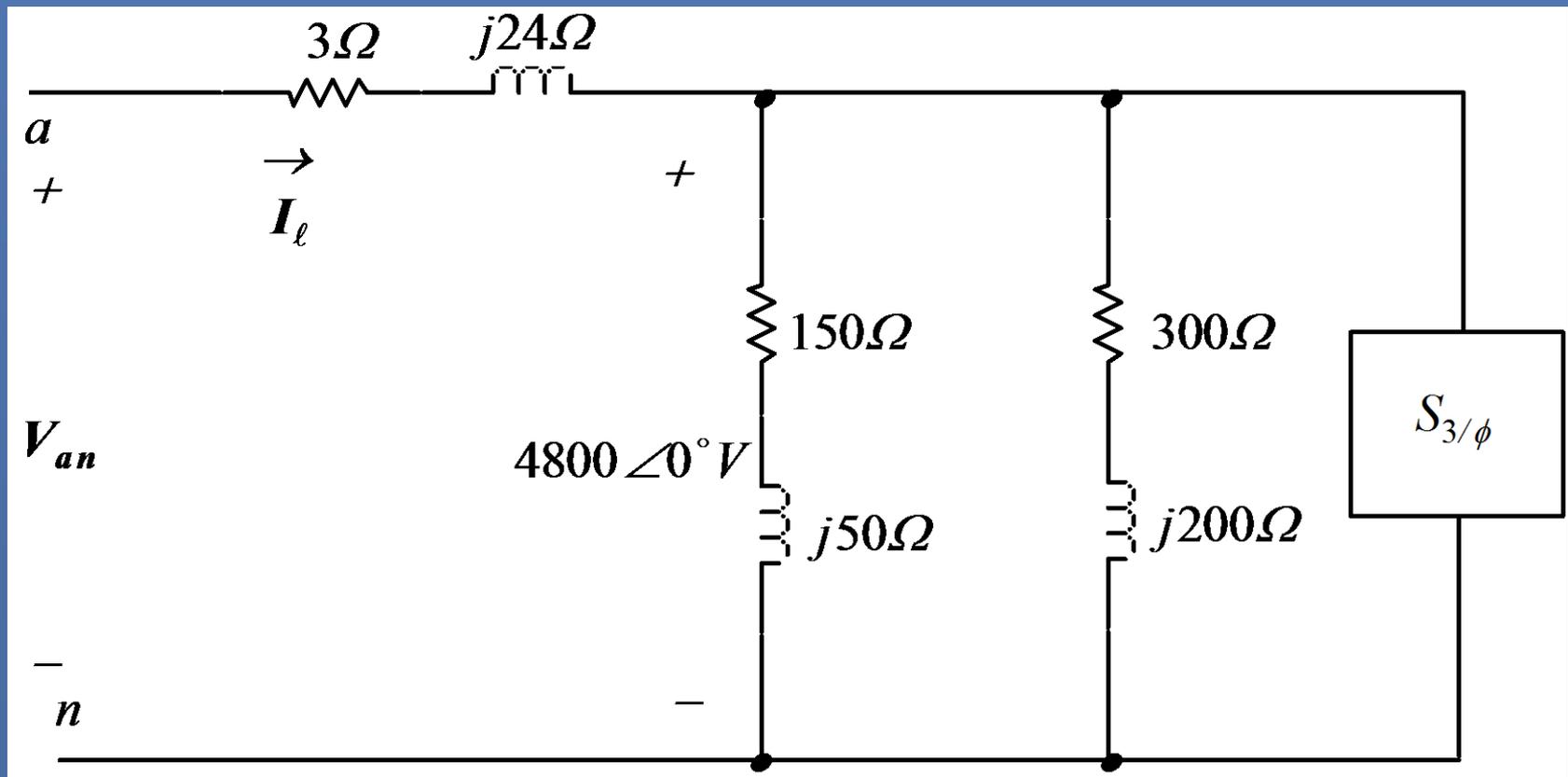

Compute current from source

$$\begin{aligned} \mathbf{I}_\ell &= \frac{4800}{150 + j50} + \frac{4800}{300 + j200} + \frac{19,008 + j25,344}{4800} \\ &= 28.8 - j9.6 + 11.0769 - j7.3846 + 3.96 + j5.28 \\ &= \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 \\ &= 43.8369 - j11.7046 \text{ A}(rms) = 45.3725 \angle -14.949^\circ \text{ A}(rms) \end{aligned}$$

Compute losses in the transmission line

$$P_{loss} = 3 |I_{eff}|^2 R = 3(45.3725)^2(3) = 18,528.04 \text{ W}$$

$$Q_{loss} = 3 |I_{eff}|^2 X = 3(45.3725)^2(24) = 148,224.34 \text{ VAR}$$

Compute power consumed by load 1.

$$P_1 = 3 |28.8 - j9.6|^2 (150) = 414,720 \text{ W}$$

$$Q_1 = 3 |28.8 - j9.6|^2 (50) = 138,240 \text{ VAR (abs)}$$

Compute power consumed by load 2:

$$P_2 = 3 \left| 11.0769 - j7.3846 \right|^2 (300) = 159,507.02 \text{ W}$$

$$Q_2 = 3 \left| 11.0769 - j7.3846 \right|^2 (200) = 106,338.02 \text{ VAR(abs)}$$

Compute power consumed by load 3:

$$P_3 = 95,040(0.6) = 57,024 \text{ W}$$

$$Q_3 = -95,040(0.8) = -76,032 \text{ VAR}$$

Add the powers to the three loads

$$S_{totalload, 3\phi} = 631,251 + j168,546 \text{ VA (load end)}$$

We could have also obtained this from $3VI^*$ (see the “check” in the text)

Add in the losses to get sending end power:

$$\begin{aligned} S_{sending, 3\phi} &= 631,251 + j168,546 + 18,528.04 + j148,224.34 \text{ VA} \\ &= 649779.04 + j316,770.34 \text{ VA} \end{aligned}$$

Part b of the problem wants the percent of the power from the sending end that is actually delivered at the load.

$$\% P \text{ delivered} = \frac{631,251}{649,779.04} \times 100 = 97.148$$

This is a measure of efficiency.

Why is 100% of the power not delivered?