## EE 303, Quiz 4, Spring 2017, Dr. McCalley

1. (30 pts) The following is a circuit model of a transformer.



Answer the following questions:

- a. What element or elements model the leakage flux?  $X_1$  and  $X_2$
- b. What element or elements model the real power losses caused by eddy currents in the transformer core?\_\_R\_\_\_
- c. What element or elements model the hysteresis losses in the transformer core?  $R_{c}$
- d. What element or elements model the real power losses caused by  $I^2R$  effect in the windings? \_\_\_\_\_R\_1 and R\_2\_\_\_\_R\_2 and R\_2\_\_\_R\_2 and R\_2\_\_R\_2 and R\_2\_\_R\_2 and R\_2\_\_R\_2 and R\_2\_\_R\_2 and R\_2\_R\_2 a
- e. What element or elements model the reactive power associated with setting up the magnetizing flux in the core?\_
- 2. (40 pts) In the circuit below, the primary turns is N<sub>1</sub>=100 and the secondary turns is N<sub>2</sub>=10. Refer all of the numerical quantities indicated over to the primary side and draw the primary-side circuit you would use for analysis. Label the resistant elements appropriately and give their valu  $V'_2$ ,  $E'_2$ ,  $I'_2$ ,  $E'_1$ ,  $I'_1$ , I'

Xm



Solution:



3. (30 pts) Consider the following circuit which is exactly the same as the one discussed in the last class. It is a per-phase circuit of a three-phase system. The three phase power consumed by load #3 is 95.04 kVA at 0.6 pf leading.



Choose your base line-to-neutral voltage as 5000volts and your base per-phase power as 100,000volt-amperes.

- a. Compute the base line current.
- b. Compute the base impedance for Y-connected loads.
- c. Compute the per-unit voltage applied at load.
- d. Compute the per-unit power consumed by load #3.
- e. Compute the per-unit impedances for the impedance of the two constant impedance loads.

## Solution:

- a.  $I_{base} = S_{1,base} / V_{LN, base} = 100,000/5000 = 20 \text{ or } I_{base} = S_{3,base} / (sqrt(3)V_{LL, base}) = 300,000/sqrt(3)sqrt(3)5000 = 20 \text{ amps.}$
- b.  $Z_{base} = V_{LN,base}/I_{base} = 5000/20 = 250$  ohms or  $Z_{base} = (V_{LL,base})^2/S_{3,base} = (sqrt(3)*5000)^2/300,000 = 250$  ohms
- c. V<sub>pu,load</sub>=4800/5000=0.96pu
- d.  $S_{3,pu}=95,040(0.6-j0.8)/300,000=0.3168(0.6-j0.8)$
- e.  $Z_{1,pu}=(150+j50)/250=(0.6+j0.2)pu; Z_{2,pu}=300+j200//250=(1.2+j0.8)pu.$