EE 303 Sample Final Exam. Time: 2 hrs. Open book, open notes. Calculator allowed. Write all answers on a separate sheet. Indicate the problem and part clearly. Number your pages.

- 1. (24) <u>3 phase circuits, synchronous generators, and power factor correction</u>: Two three-phase balanced loads are connected in parallel directly to a balanced synchronous generator with positive (a-b-c) phase sequence. Load #1 is Y-connected with impedance 100+j50 ohms/phase. Load #2 is Δ -connected with impedance 300-j180 ohms/phase. The line-to-neutral voltage of the supply is 277 volts. Assume V_{an} is the reference, i.e., V_{an}=277 $\angle 0^\circ$. Denote E_{an} as the line-to-neutral internal voltage of the synchronous generator, and δ is its angle.
 - a. What is V_{ab} (magnitude and angle)?
 - b. Compute I_{an} for the Y-connected load (magnitude & angle) and its power factor (leading/lagging).
 - c. Compute I_{ab} for the Δ -connected load (magnitude & angle) and its power factor (leading/lagging).
 - d. Compute the supply current from the synchronous generator I_a (magnitude and angle).
 - e. What is the power factor of the composite load (leading/lagging)?
 - f. How much complex power is produced by the synchronous generator?
 - g. Under this condition, which quantity is larger, $|\mathbf{E}_{an}|\cos\delta$ or $|\mathbf{V}_{an}|$?
 - h. How many vars need to be provided at the load to bring the power factor to 1.0?
- (23) <u>Power flow</u>: A 3-bus system has a generator and load at each bus. The numbers given beside each branch are admittances. There is no line charging represented. Denote the injections as P_k, Q_k, the corresponding power flow equations as P_k(<u>x</u>), Q_k(<u>x</u>), and the voltage phasors at each bus as V_k∠δ_k, where k=1,2,3. Assume δ₁=0°.

a. (6) Write down the Y-bus matrix.

b. (5) Identify the variables in the solution vector.



- c. (6) It is possible to write a power flow equation for real and reactive injections at buses 1, 2, and 3 (giving a total of 6 equations). From these six equations, write down the mismatch equation(s) that are required in the solution procedure. Express each equation symbolically (no numbers) in terms of P_k , Q_k , $P_k(\underline{x})$, $Q_k(\underline{x})$, k=1,2,3. Denote each equation by $g_i(\underline{x})$.
- d. (6) Write down the Jacobian matrix <u>J</u> used in the solution procedure. Indicate elements in the matrix using partial derivative notation; you need not differentiate anything or provide numerical values.
- 3. (18) Optimization: (18 pts) A small power system has only two generation units. The derivatives of the cost-rate functions for the two units are as follows:

 $dC_1/dP_1=2P_1+2$, $dC_2/dP_2=3P_2+4$ (in \$/MWhr for both derivative functions) Unit 1 can supply from 0 to 9 MW and unit 2 can supply from 0 to 11 MW.

- a. (2) When the load is 10 MW, the output at the two plants is set at 5 MW for both unit 1 and unit 2. What is the incremental cost of each unit at this dispatch?
- b. When the load is 10 MW, the units are dispatched optimally (so as to minimize the total cost rate).
 - i. (2) What is the optimal dispatch?
 - ii. (2) What is the incremental cost of each unit at this dispatch?
 - iii. (2) What is the system lambda at this dispatch?
- c. (4) How much would the objective function change if the load increased from 10 MW to 11 MW, assuming the dispatch was kept optimal.
- d. (6) When the load is 20 MW, the optimal solution in the first step of the solution procedure (ignoring inequality constraints) is P₁=12.4MW, P₂=7.6MW, λ=26.8\$/MWhr. In the second step, the solution is found to be P₁=9MW, P₂=11MW, λ=37\$/MWhr, μ₁=-17\$/MWhr.
 - i. Only one inequality constraint is "mathematically" binding. Which one is it?
 - ii. For this 20 MW load, how much would the objective function change if the unit 1 upper limit was increased to 10 MW, assuming the dispatch was kept optimal?
 - iii. For this 20 MW load, how much would the objective function change if the upper limit of unit 2 was increased to 12 MW, assuming the dispatch was kept optimal?
- 4. (21 pts) Short answer:
 - a. What is the essential control parameter in using a BJT as a controlled switch?
 - b. What two regions does a BJT operate in when serving as a controlled switch?
 - c. What is the essential control parameter in using a naturally commutated thyristor as a controlled switch?
 - d. What is the main operational difference between a thyristor and a diode?
 - e. Why is energy dissipation used in controlled switching a motor?
 - f. What is the advantage of energy recovery over energy dissipation?
 - g. What are the three control parameters for performing speed control for a DC motor?
- 5. (14 pts) True-false:
 - a. An induction motor is like a transformer in that the voltage of one of the windings is induced.
 - b. Induction motors are like synchronous machines in that both have externally supplied field windings.
 - c. An induction motor is like a DC motor in that both devices have AC applied to 3 stator windings.
 - d. Rotor speed for an induction motor is fixed whereas rotor speed for a synchronous machine varies.
 - e. A slip of 0 corresponds to a stationary rotor.
 - f. A DC motor is like a synchronous machine in that both may utilize slip rings and brushes.
 - g. It is common to perform power factor correction by controlling field current of an induction motor.