

Datapath & Control Design

- We will design a simplified MIPS processor
- The instructions supported are
 - memory-reference instructions: `lw`, `sw`
 - arithmetic-logical instructions: `add`, `sub`, `and`, `or`, `sll`
 - control flow instructions: `beq`, `j`
- Generic Implementation:
 - use the program counter (PC) to supply instruction address
 - get the instruction from memory
 - read registers
 - use the instruction to decide exactly what to do
- All instructions use the ALU after reading the registers
 - Why? memory-reference? arithmetic? control flow?

1


What blocks we need

- We need an ALU
 - We have already designed that
- We need memory to store inst and data
 - Instruction memory takes address and supplies inst
 - Data memory takes address and supply data for `lw`
 - Data memory takes address and data and write into memory
- We need to manage a PC and its update mechanism
- We need a register file to include 32 registers
 - We read two operands and write a result back in register file
- Some times part of the operand comes from instruction
- We may add support of immediate class of instructions
- We may add support for `J`, `JR`, `JAL`

2

Simple Implementation

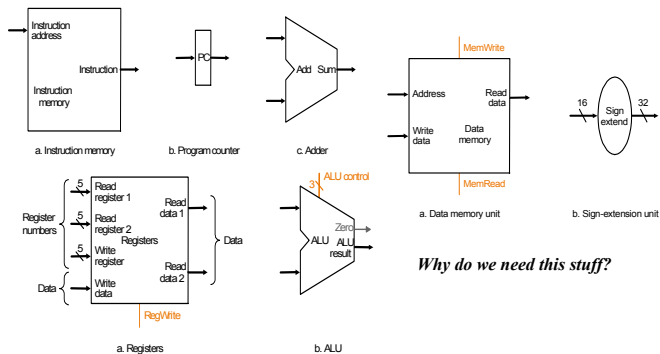
- Include the functional units we need for each instruction



3

More Implementation Details

- Abstract / Simplified View:

 


- Two types of functional units:
 - elements that operate on data values (combinational)
 - Example: ALU
 - elements that contain state (sequential)
 - Examples: Program and Data memory, Register File

4

Managing State Elements

 
- Unclocked vs. Clocked
- Clocks used in synchronous logic
 - when should an element that contains state be updated?



5

Building the Datapath

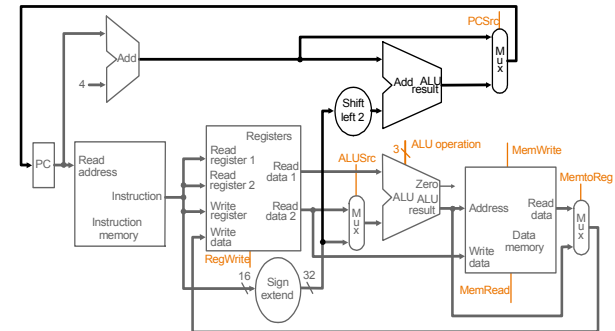- Use multiplexors to stitch them together



6

Latches and Flip-flops


- Output is equal to the stored value inside the element
 - (don't need to ask for permission to look at the value)
 - "logically true" could mean electrically low
- Change of state (value) is based on the clock
- Latches: whenever the inputs change, and the clock is asserted
- Flip-flop: state changes only on a clock edge (edge-triggered methodology)

A clocking methodology defines when signals can be read and written
 — wouldn't want to read a signal at the same time it was being written

7

An unlocked state element

 
- The set-reset latch
 - output depends on present inputs
 - If present inputs are 00, then it depends on the past inputs
 - What happens if R=1, S=1?



8

D-latch

 
- **Two inputs:**
 - the data value to be stored (D)
 - the clock signal (C) indicating when to read & store D
- **Two outputs:**
 - the value of the internal state (Q) and its complement



9

D flip-flop

 
- **Output changes only on the clock edge**



10

Our Implementation

 
- **An edge triggered methodology**
- **Typical execution:**
 - read contents of some state elements,
 - send values through some combinational logic
 - write results to one or more state elements



11

Register File

- **Built using D flip-flops**

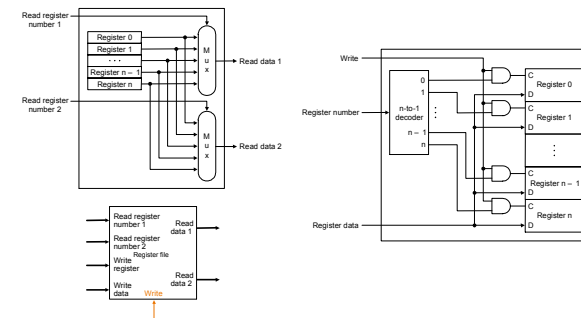

12

Data Path Composition

Data paths for inst classes

1. Arithmetic-logic
2. Memory references
3. Branch and Jump


Data path stages

- Instruction fetch
- Read operands
- ALU operation
- Memory access
- Register write
- PC Update

13

Instruction Fetch

 
- PC determines the next instruction to fetch (and to execute)
- Branch and jump changes PC



14

Datapath for R-type Instructions

 
1. Instruction fetch
2. Read registers: for the two source operands
3. ALU: perform the arithmetic-logic operation
4. Write register: to the destination register



15

Datapath for Memory Reference Instructions

 
1. Instruction fetch
2. Read registers: base address and data (for load)
3. ALU: calculating effective address
4. Memory access: read/write data
5. Write register (for store)



16

Datapath for Branch Instructions

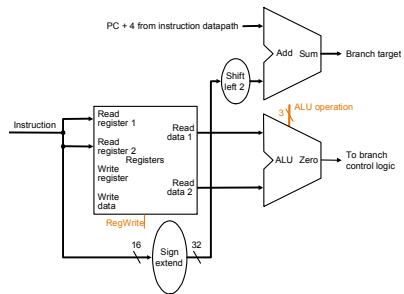
1. Instruction fetch
2. Read registers: two operands in beq
3. ALU: compare two operands
4. Update PC



17

A Complete Datapath for Core Instructions

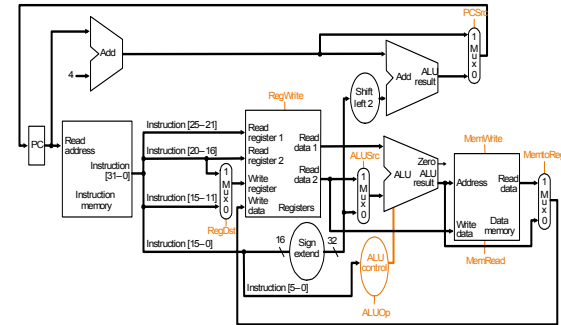- Supports Lw, Sw, Add, Sub, And, Or, Slt, and Beq
- All control lines identified



18


What Else is Needed in Datapath

- Support for j and jr
 - For both of them PC value need to come from somewhere else
 - For J, PC is created by 4 bits (31:28) from old PC, 26 bits from IR (27:2) and 2 bits are zero (1:0)
 - For JR, PC value comes from a register
- Support for JAL
 - Address is same as for J inst
 - OLD PC needs to be saved in register 31
- And what about immediate operand instructions
 - Second operand from instruction, but without shifting
- Support for other instructions like lw and immediate inst write

19

Single-cycle Implementation

 
- Execute every instruction in one cycle
 - Simple implementation with simple control
- We wait for everything to settle down, and the right thing to be done
 - ALU might not produce “right answer” right away
 - We use write signals along with clock to determine when to write
 - No single element can be used twice
- Cycle time determined by length of the longest path



We will study more clever implementation

20

Adding Control to Datapath

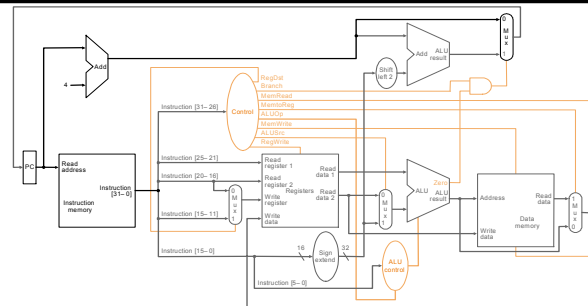

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUOp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

21

Main Control Descriptions

Signal name	When deasserted	When asserted
RegDst	Dest reg number \leftarrow \$rt	Dest reg number \leftarrow \$rd
RegWrite		Write register
ALUSrc	2nd ALU input \leftarrow \$rt	2nd ALU input \leftarrow I-field
PCSrc (Branch)	PC \leftarrow PC+4	PC \leftarrow address ALU output
MemRead		Enable data memory read
MemWrite		Enable data memory write
MemtoReg	Reg data \leftarrow main ALU output	Reg data \leftarrow data memory

Q: What determines the values of those signals?

22